

Electric Circuits

Answer Sheet – Homework Set 10

Questions beginning with ** do not have answers on this sheet.

NOTE! *It is possible your answers for current could have a different sign depending on how you draw or your label circuits where you have a choice.*

0.727 V

2 μ W

0.727 mA

2.7 V

-0.1 μ V

2

-2.4

10 μ A

-9.9988 mV

-5

2.7 V

-16

-400

0.288 mA

-0.5625 mA