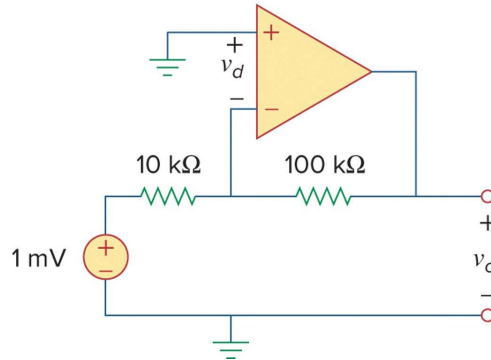


Electric Circuits


Homework Set 10

Except for the one in problem 1, assume all other op amps are ideal.


- The op amp below has $R_i = 100 \text{ k}\Omega$, $R_o = 100 \text{ }\Omega$, $A = 100,000$. Find the differential voltage, v_d , and the output voltage, v_o .



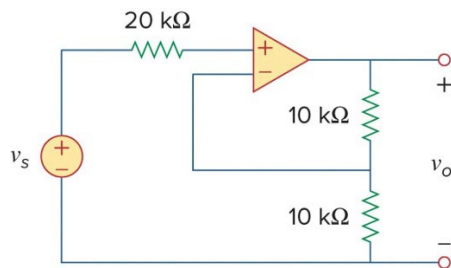
- Find the gain v_o/v_s of the following circuit.



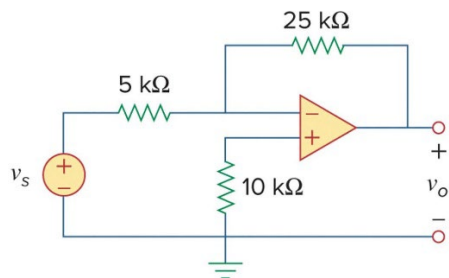- Calculate the voltage ratio v_o/v_s for the op amp circuit below.




- Find v_o and i_o in the circuit below.

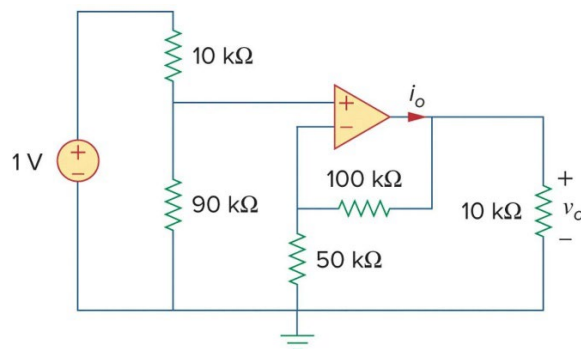


5. Calculate the gain v_o/v_i when the switch in the following circuit is in:


- Position 1
- Position 2
- Position 3

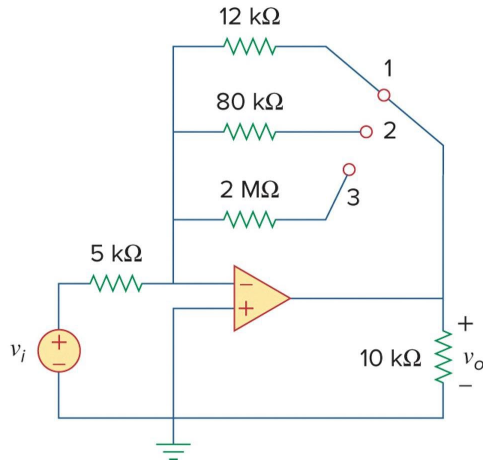


6. Determine i_o in the circuit below.

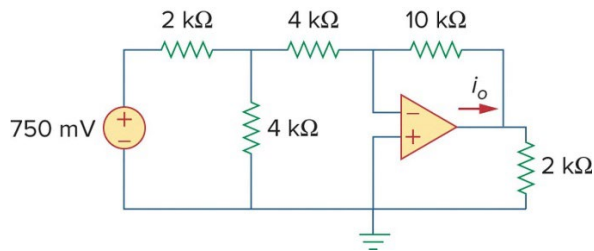

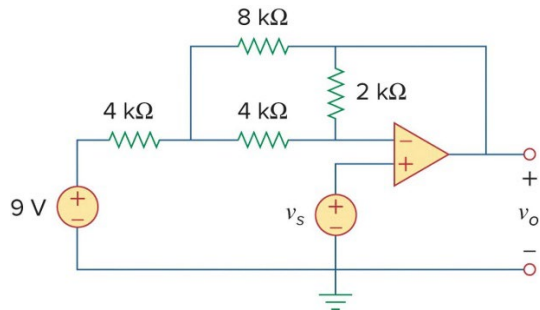
7. In the circuit below, calculate v_o if $v_s = 2$ V.



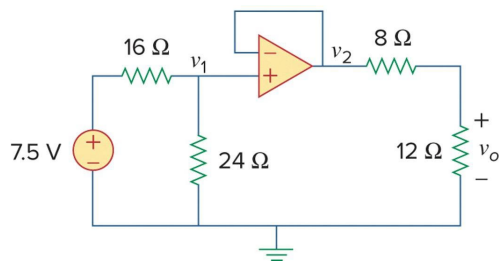
8. Find v_o in the op amp circuit that follows.



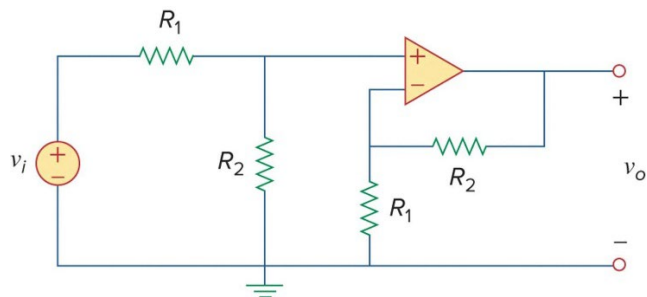9. **Determine the voltage gain v_o/v_i of the op amp circuit in the circuit below.



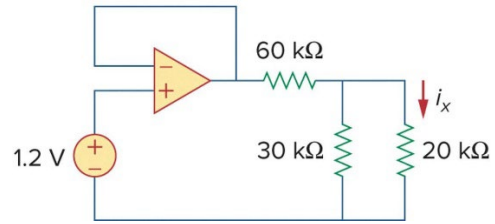10. In the circuit shown, find i_x and the power absorbed by the $20\text{ k}\Omega$ resistor.



11. For the circuit below, find i_x .

