

## Electric Circuits

### Answer Sheet – Homework Set 11

Questions beginning with \*\* do not have answers on this sheet.

**NOTE!** *It is possible your answers for current could have a different sign depending on how you draw or label circuits where you have a choice.*

-4.5 V

7.5 V

3 V

0.151 mA

14.1 V

1.5 V

0.685 mA

0.667 V

-4 V

-6.7 mV