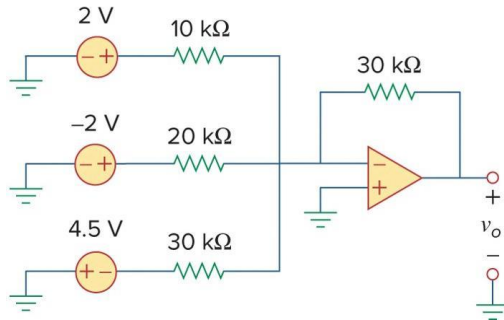



Electric Circuits

Homework Set 11


- Determine the output of the summing amplifier shown below.



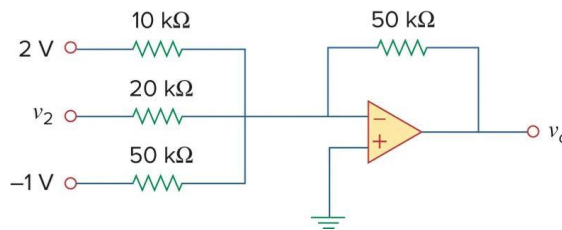
- For the op-amp circuit below, determine the value of v_2 in order to make $v_o = -16.5$ V



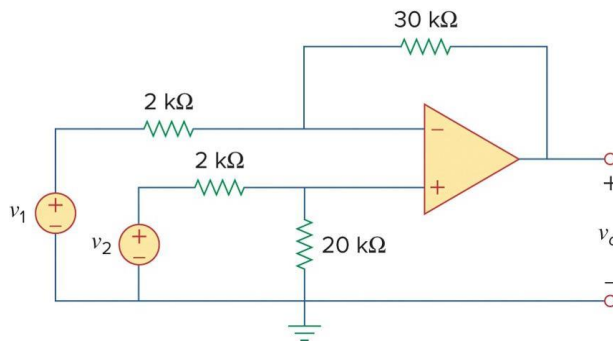
- The following circuit is for a difference amplifier. Find v_o given that $v_1 = 1$ V and $v_2 = 2$ V.



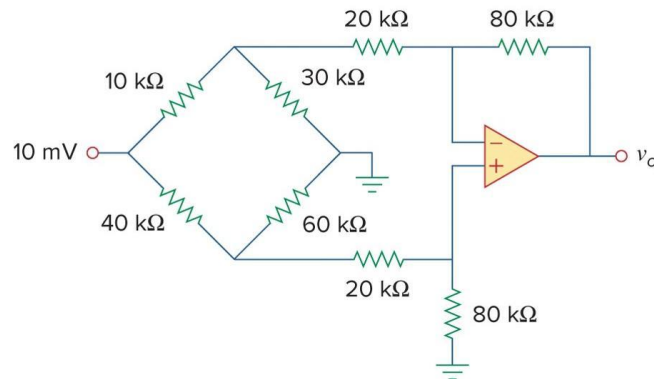
- The circuit below is a differential amplifier driven by a Wheatstone bridge. Find v_o .



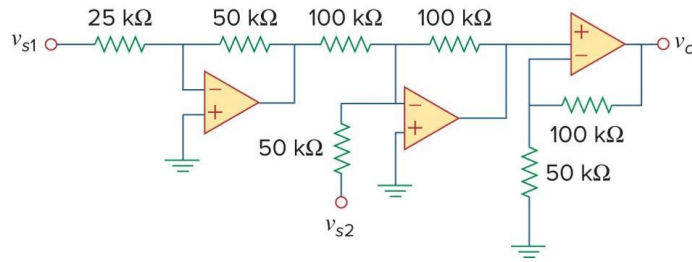
5. **Find an expression for v_o in terms of v_{s1} and v_{s2} in the op-amp circuit below.



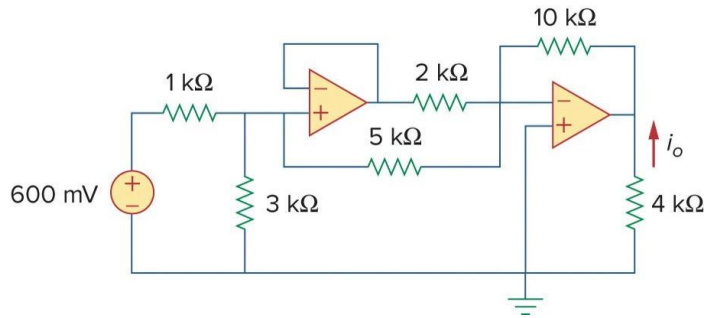
6. Calculate i_o in the following op-amp circuit.



7. For the circuit below, find v_o .

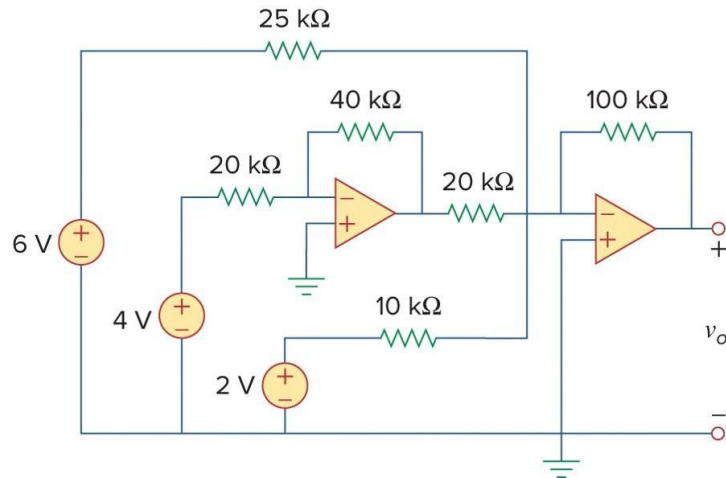


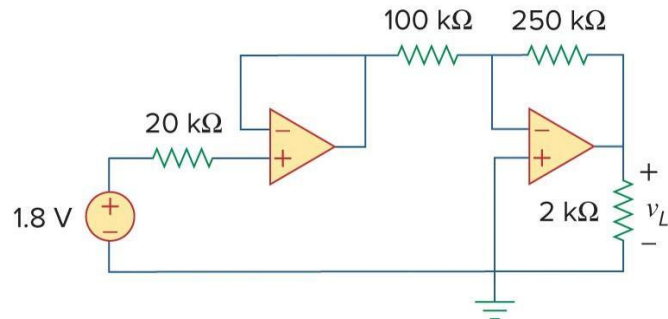8. Find the load voltage v_L in the following circuit.




Use Micro-Cap or Multisim to solve the following circuits. **Be sure to print out your results to turn in.**

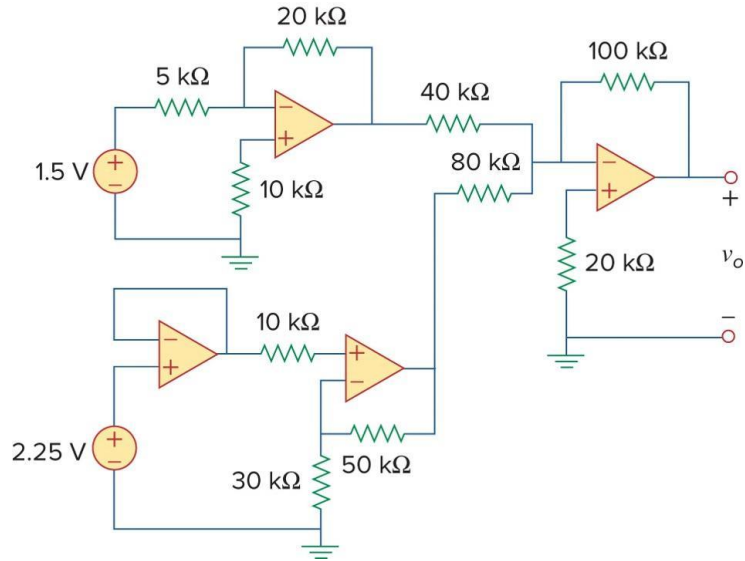9. Evaluate the following circuit to find v_o .



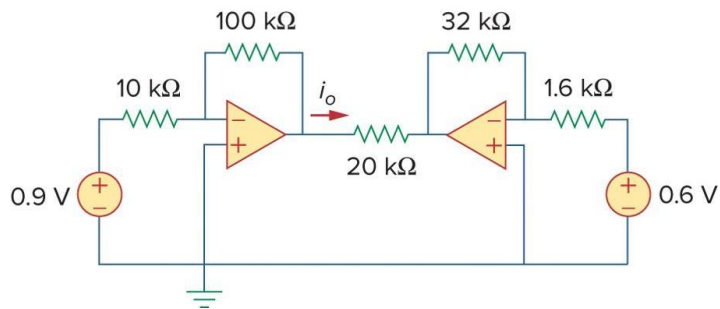10. Evaluate the following circuit to find i_o .



11. Evaluate the circuit below to find v_o .

