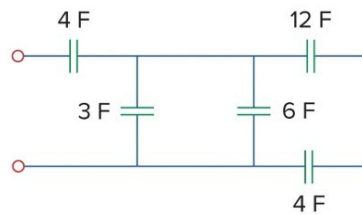



Electric Circuits

Homework Set 12


1. If the voltage across a 7.5 F capacitor is $2te^{-3t}$ V, find the current and the power.
2. A current of $4\sin(4t)$ (in amps) flows through a 5 F capacitor. Find the voltage $v(t)$ across the capacitor given that $v(0) = 1$ V.
3. The current through a 0.5 F capacitor is $6(1 - e^{-t})$ A. Determine the voltage and power at $t = 2$ s. Assume $v(0) = 0$.
4. Determine the equivalent capacitance for each of the following circuits.



(a)

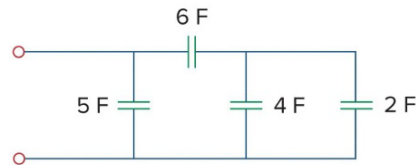


(b)

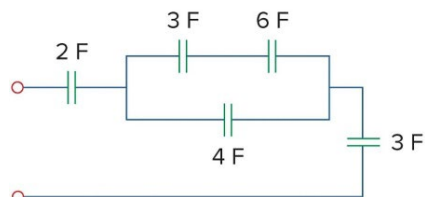


(c)

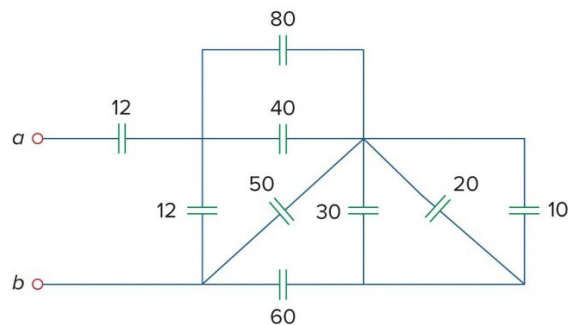5. Find the equivalent capacitance between the terminals a and b in the circuit below. (All capacitances are in μF).



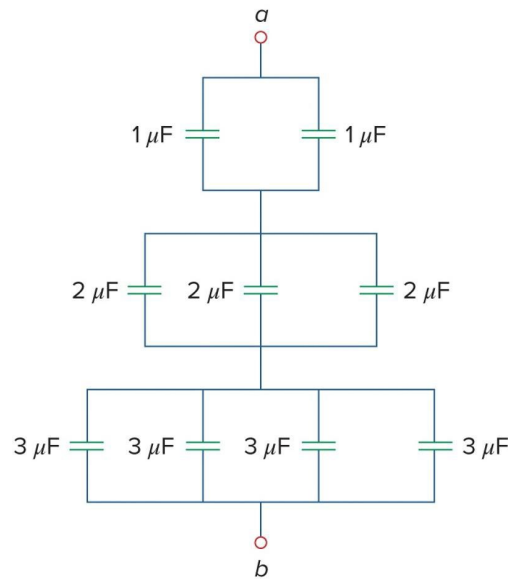6. Find the equivalent capacitance at terminals a - b of the following circuit.




7. In the circuit shown below,


$$v(t) = 56e^{-200t}\ \text{V},\ t > 0$$

$$i(t) = 8e^{-200t}\ \text{mA},\ t > 0$$

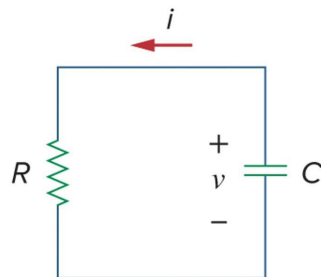
- Find the values of R and C
- Calculate the time constant τ
- Determine the time required for the voltage to decay to half of its original value at $t = 0$.



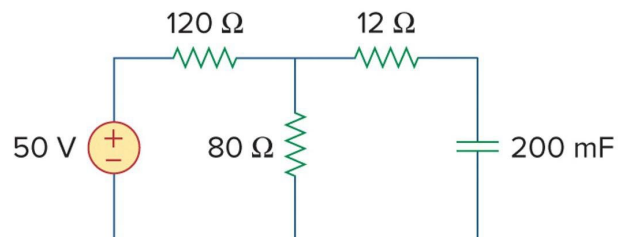
8. Find the time constant for the following RC circuit.



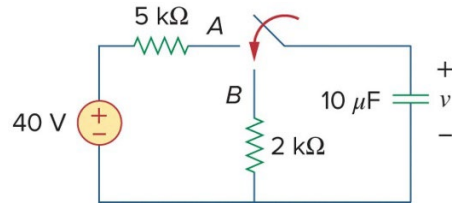9. The switch in the circuit below has been in position A for a long time. Assume the switch moves instantaneously from A to B at $t = 0$. Find v for $t > 0$.



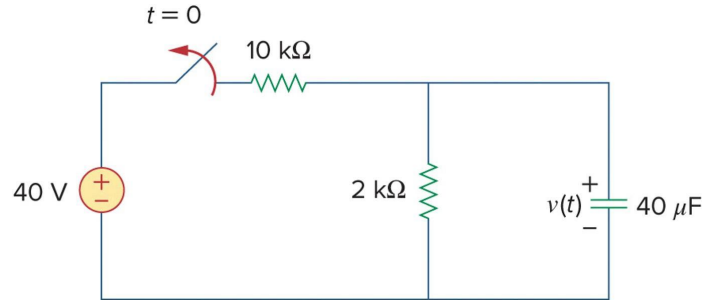10. The switch in the following circuit has been closed for a long time, and it opens at $t = 0$. Find $v(t)$ for $t \geq 0$.




11. In the circuit shown below,


$$v(t) = 10e^{-4t} \text{ V}, \quad t > 0$$

$$i(t) = 0.2e^{-4t} \text{ A}, \quad t > 0$$

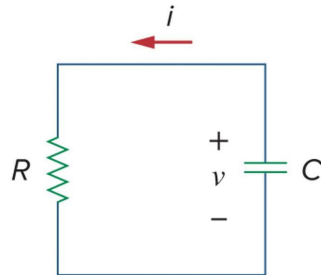
- Find R and C
- Determine the time constant τ
- Calculate the initial energy in the capacitor
- Obtain the time it takes to dissipate 50% of the initial energy



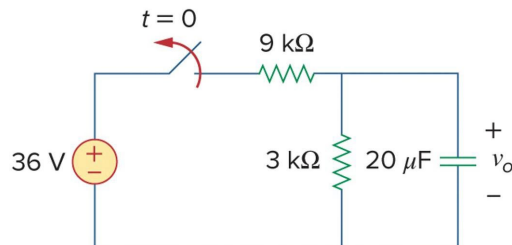
12. For the following circuit, find $v_o(t)$ for $t > 0$. Determine the time necessary for the capacitor voltage to decay to $1/3$ of its original value at $t = 0$.



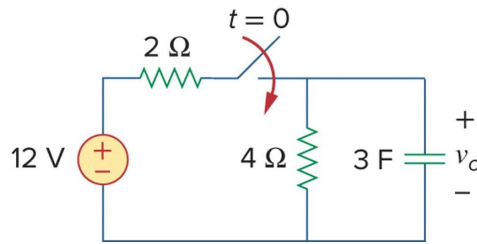13. (a) If the switch in the circuit below has been open for a long time and is closed at $t = 0$. Find $v_o(t)$.
 (b) Suppose the switch has been closed for a long time and is opened at $t = 0$. Find $v_o(t)$.



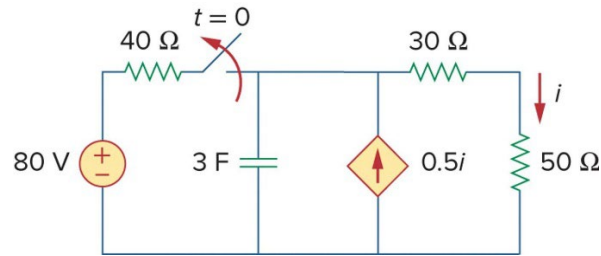14. Consider the circuit shown below. Find $i(t)$ for $t < 0$ and $t > 0$.



15. The switch in the following circuit has been in position a for a long time. At $t = 0$, it moves to position b. Calculate $i(t)$ for all $t > 0$.

