

Electric Circuits

Answer Sheet – Homework Set 3

Questions beginning with ** do not have answers on this sheet.

0.2 A

45 A

-1.2 A

0.6 V

22410 W

73 Ω

- 4.8 A

4

- 6 A

7.5 Ω

3.5 A

4 Ω

5.82 Ω

2.5 A

10 Ω

240 Ω

0.184 m

0.4 A

0.16 A

6

100 Ω

- 4 A

2 Ω

400 W

1.5 A