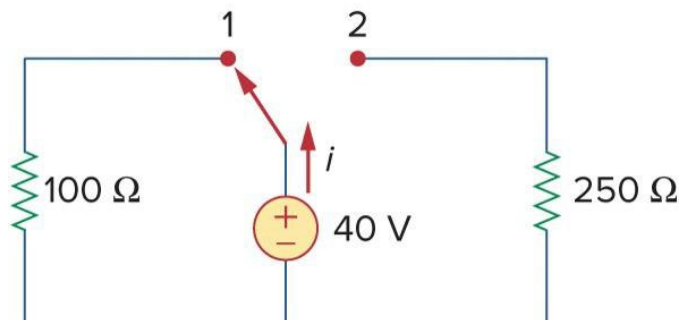



## Electric Circuits

### Homework Set 3


1. Find the hot resistance of a light bulb rated 60 W, 120 V.
2. A bar of silicon is 4 cm long with a circular cross section. If the resistance of the bar is  $240\ \Omega$  at room temperature, what is the cross-sectional radius of the bar? (Note:  $\rho_{\text{silicon}} = 640\ \Omega\ \text{m}$ )
3. For the following circuit,
  - a. Calculate the current when the switch is in position 1.
  - b. Calculate the current when the switch is in position 2.



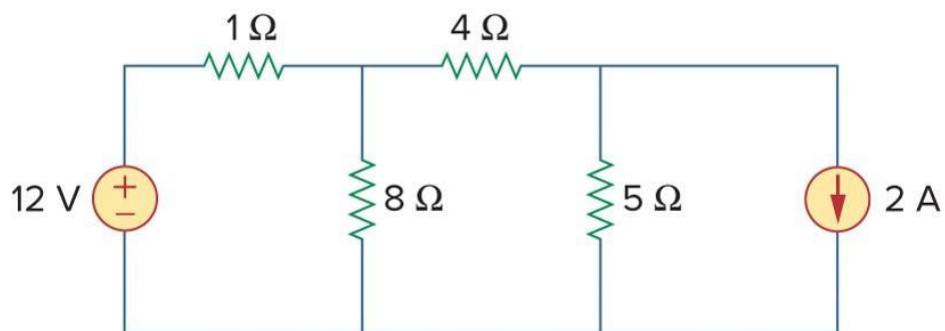
4. Determine the number of branches and nodes in the following circuit.



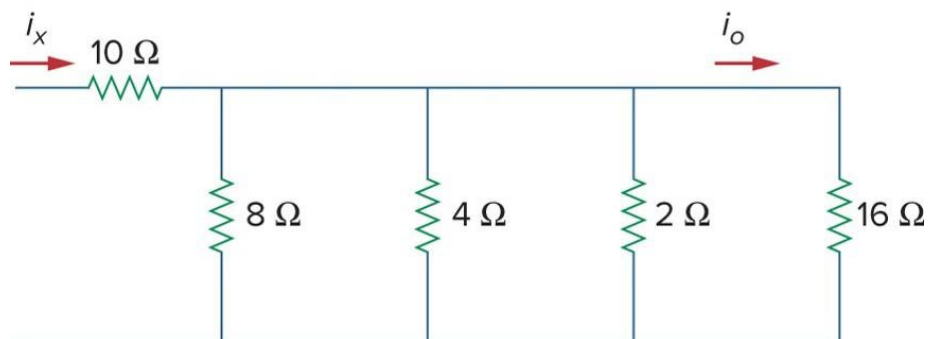
5. In the following circuit,  $i_o = 3\ \text{A}$ . Calculate  $i_x$  and the total power absorbed by the entire circuit.



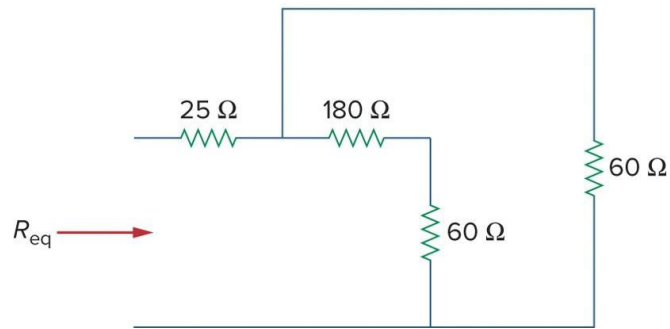
6. Find  $R_{eq}$  for the following circuit.



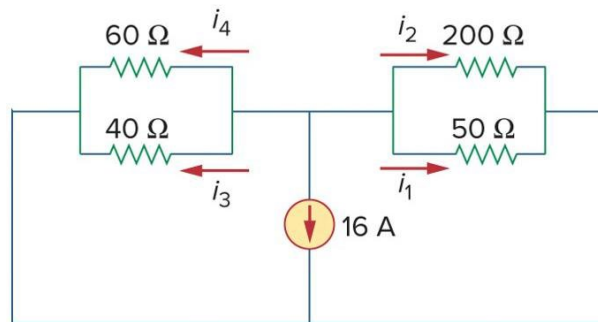
7. For the circuit below, find  $i_1$  through  $i_4$ .



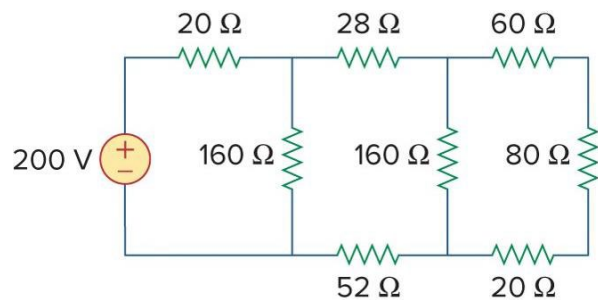
8. Using series/parallel resistance combination, find the equivalent resistance seen by the source in the following circuit. Use this value to determine the overall absorbed power by the resistor network.



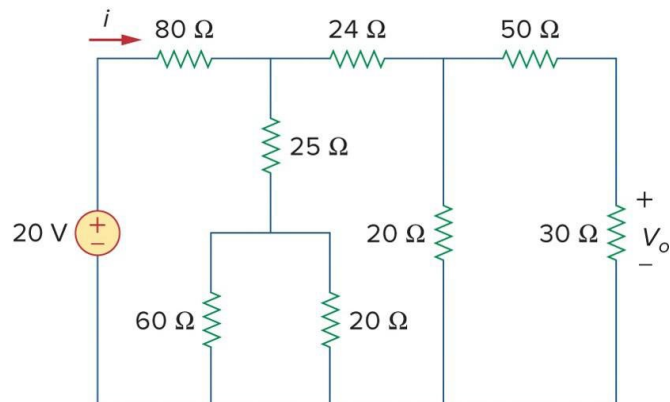
9. Find  $i$  and  $V_o$  in the circuit below.



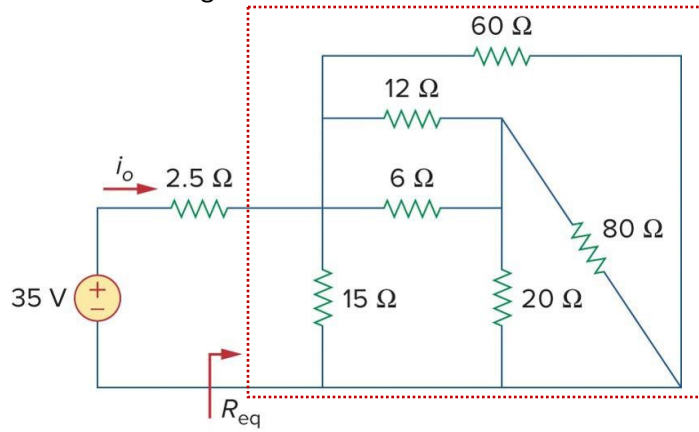
10. Find  $R_{eq}$  and  $i_o$  in the following Circuit.



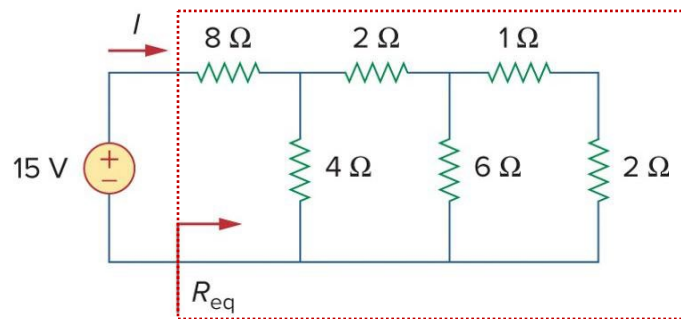
11. For the ladder network below, find  $I$  and  $R_{eq}$ .



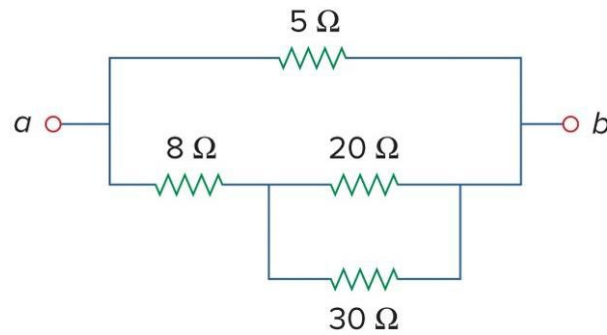12. Reduce each of the following circuits to a single resistor between terminals  $a$ - $b$ .




(a)

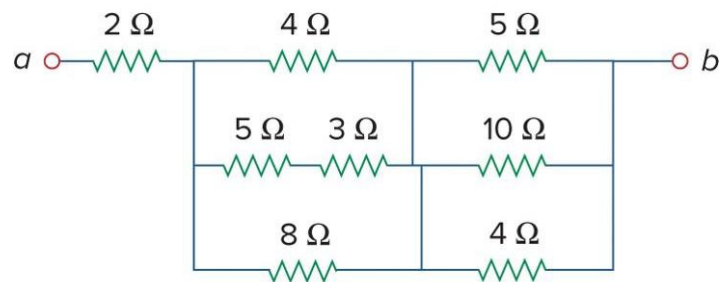

(b)

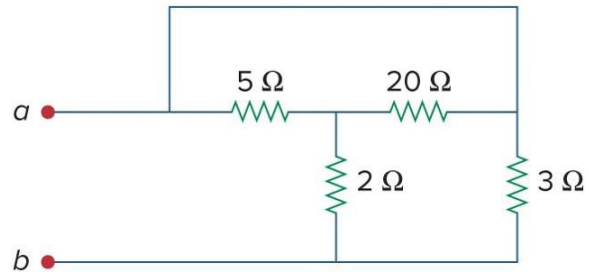13. For the circuit below, obtain the equivalent resistance at terminals a-b.



14. Find  $I$  in the following circuit.

