

## Electric Circuits

### Answer Sheet – Homework Set 4

Questions beginning with \*\* do not have answers on this sheet.

9.22  $\Omega$

142.3  $\Omega$

9.23  $\Omega$

155  $\Omega$

0.996 A

42.2 V

1.64 A

12.2  $\Omega$

62  $\Omega$

130  $\Omega$

103.3  $\Omega$

18  $\Omega$

3  $\Omega$

6  $\Omega$

140  $\Omega$

4  $\Omega$

30  $\Omega$

36.25  $\Omega$

33.3  $\Omega$