

Electric Circuits

Answer Sheet – Homework Set 5

Questions beginning with ** do not have answers on this sheet.

NOTE! *It is possible your answers for current could have a different sign depending on how you draw your current direction on circuits where you have a choice.*

2 A

4.17 V

4 Ω

0.8 Ω

-4 A

30 W

3.33 k Ω

18 V

2 V

1.18 Ω

-20 W

6 V

-16 W

75 Ω

-22 V

-2 A

12 W

24 W

38 k Ω

10 V

4 A

28 V