

## Electric Circuits

### Answer Sheet – Homework Set 6

Questions beginning with \*\* do not have answers on this sheet.

**NOTE!** *It is possible your answers for current could have a different sign depending on how you draw or your label circuits where you have a choice.*

-7.2 V

-2.8 V

4.85 V

-4 A

-4.5 A

-1075.2 V

4.97 V

60 V

-3 V

4.5 V

-15 V

-10.9 V

12.3 V

12 V

50 V

30 V

-43.8 V

20.6 V

1.4 V

60 V

-100.4 V

1.6 V

-0.12 V

2.9 V

-10.6 V

60 V