

## Electric Circuits

### Answer Sheet – Homework Set 7

Questions beginning with \*\* do not have answers on this sheet.

**NOTE!** *It is possible your answers for current could have a different sign depending on how you draw or your label circuits where you have a choice.*

-0.476 A

0.49 A

2.94 V

-3.625 A

0.0025 mA

-26 A

-2.233 A

2 A

2.25 A

-0.278 A

-1.049 A

8 mA

1.188 A

1.778 A

53.3 V

8.56 A

2.17 A

1.99 A

1.81 A

2.09 A

-1 A

0

1.468 A

2.5 V