

Electric Circuits

Answer Sheet – Homework Set 8

Questions beginning with ** do not have answers on this sheet.

NOTE! *It is possible your answers for current could have a different sign depending on how you draw or your label circuits where you have a choice.*

1.8 A

8.7 V

11.2 V

4.15 V

18 V

2 A

0.255 A

555.6 mA

- 48 V