

# Mesh Current Method

The mesh current method uses KVL, but writes all the voltages in terms of currents.

1. Draw a current loop for all available meshes in the circuit and then label each mesh current ( $i_1, i_2, \dots$ ).

→ Typically, mesh currents are drawn in a clockwise direction for consistency

2. Apply KVL around each mesh current loop for which the current is unknown.

→ Be mindful of the sign convention for currents traversing a voltage source.

3. Rewrite each unknown voltage in terms of mesh currents using Ohm's law ( $\Delta V = IR$ ).

→ The net current through a branch will be either: the mesh current only, the sum of two mesh currents or the difference of two mesh currents.



4. Solve the system of equations to get the mesh currents.
5. Use the mesh currents to find the appropriate unknown(s).

**NOTE:** Steps 2 & 3 can be done simultaneously once you become familiar with the mesh current method.