

Node Voltage Method

The node voltage method uses KCL, but writes all the currents in terms of voltages.

1. Redraw the circuit in a more logical fashion to better identify the node voltages.
2. Choose a node to be the reference node or **ground** ($V = 0$) and label all the remaining node voltages (V_1, V_2, \dots).
 - *The best choice for reference node is the essential node with the most branches connected*
3. Apply **KCL** at each node for which $V \neq 0$.
 - *All unknown currents are assumed to be positive and leaving the node*
4. Rewrite each unknown current in terms of voltage using Ohm's law ($\Delta V = IR$).
5. Solve the system of equations to get the node voltages.
6. Use the node voltages to find the appropriate unknown(s).

NOTE: Steps 3 & 4 can be done simultaneously once you become familiar with the node-voltage method.