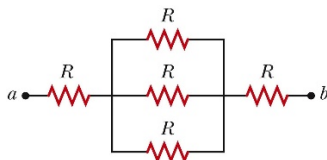



## University Physics II
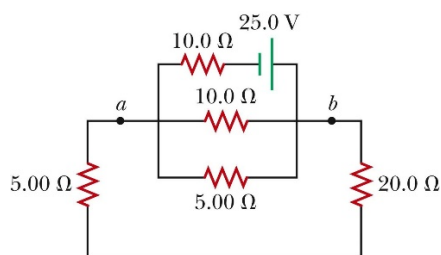
### Homework Set 6


- What is the equivalent resistance of the combination of identical resistors between points  $a$  and  $b$  in the figure below?




- Consider the circuit shown below. Find:
  - The potential difference ( $V_{ab}$ ) between points  $a$  and  $b$
  - The current in the  $20.0\ \Omega$  resistor




- You need a  $45\ \Omega$  resistor, but the stockroom only has  $20\ \Omega$  and  $50\ \Omega$  resistors. How can you combine these resistors to achieve the desired resistance?
  - What combination would you need to do if you required a  $35\ \Omega$  resistor?
- Consider the combination of resistors shown in the figure below.
  - Find the equivalent resistance between points  $a$  and  $b$ .
  - If a voltage of  $35.0\ \text{V}$  is applied between points  $a$  and  $b$ , find the current in each resistor.

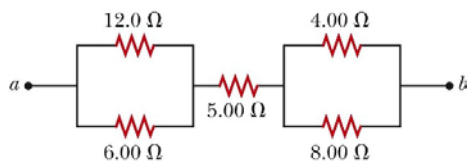

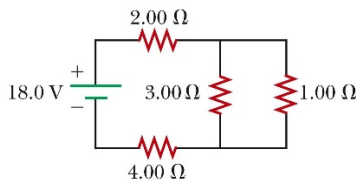
- Calculate the power delivered to each resistor in the circuit shown below.



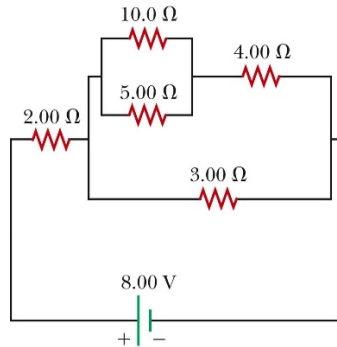
6. Consider the circuit shown below.
- Find the voltage across the  $3.00\ \Omega$  resistor
  - Find the current in the  $3.00\ \Omega$  resistor



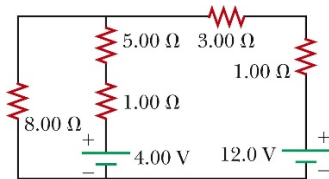
7. Consider the circuit shown below:
- Determine the current in each branch of the circuit.
  - Determine the power supplied by each battery.



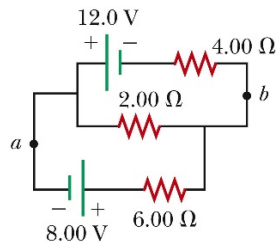8. For the circuit shown below, calculate:
- The current in the  $2.00\ \Omega$  resistor
  - The potential difference ( $V_{ab}$ ) between points  $a$  and  $b$




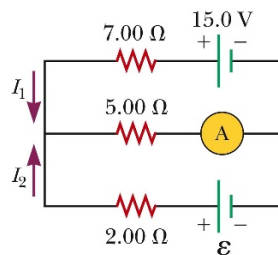9. The ammeter shown in the circuit below reads  $2.00\ \text{A}$ . Find:
- $I_1$
  - $I_2$
  - $\mathcal{E}$



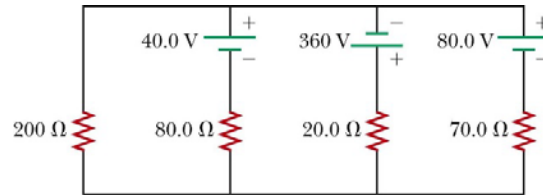
10. In the circuit below, determine:

- The current in each resistor
- The potential difference across the  $200\ \Omega$  resistor




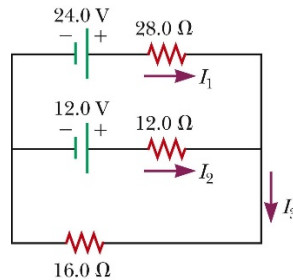11. In the circuit below, find:

- The current in each resistor
- The power delivered to each resistor



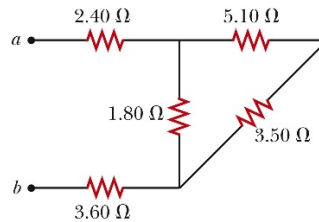12. Find the equivalent resistance between points  $a$  and  $b$  in the following figure:



13. In the circuit below, find:

- The equivalent resistance of all the resistors
- The potential difference ( $\Delta V$ ) across each resistor
- The value of each current indicated
- The power delivered to each resistor

